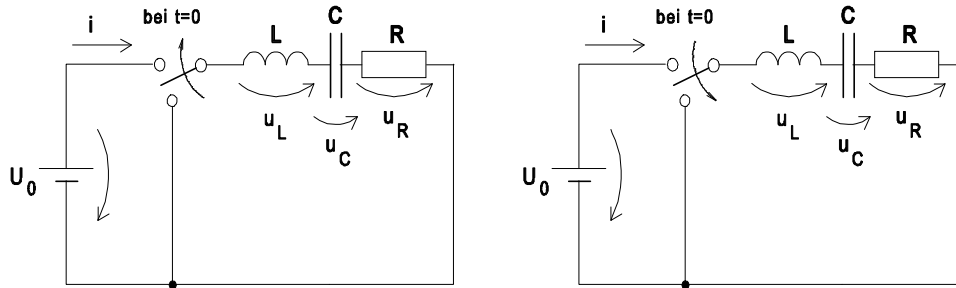


Schaltung des Reihenschwingkreises:

$L=300\text{ mH}$, $C=0,22\text{ }\mu\text{F}$, $R=300, 1600\text{ und }5000\text{ }\Omega$ bei $U_0=10\text{ V}$



1. Periodischer Fall ($R=300\text{ }\Omega$)

Theorie:

$$i = \frac{U_0}{\omega_e L} \sin \omega_e t e^{-\delta t}$$

$$u_R = \frac{U_0 R}{\omega_e L} \sin \omega_e t e^{-\delta t}$$

$$u_L = U_0 \left(\cos \omega_e t - \frac{\delta}{\omega_e} \sin \omega_e t \right) e^{-\delta t}$$

$$u_C = U_0 - U_0 \left(\cos \omega_e t + \frac{\delta}{\omega_e} \sin \omega_e t \right) e^{-\delta t}$$


mit $\delta = R/2L$, $\omega_0^2 = 1/LC$ und $\omega_e^2 = \omega_0^2 - \delta^2$


$$i = -\frac{U_0}{\omega_e L} \sin \omega_e t e^{-\delta t}$$

$$u_R = -\frac{U_0 R}{\omega_e L} \sin \omega_e t e^{-\delta t}$$

$$u_L = -U_0 \left(\cos \omega_e t - \frac{\delta}{\omega_e} \sin \omega_e t \right) e^{-\delta t}$$
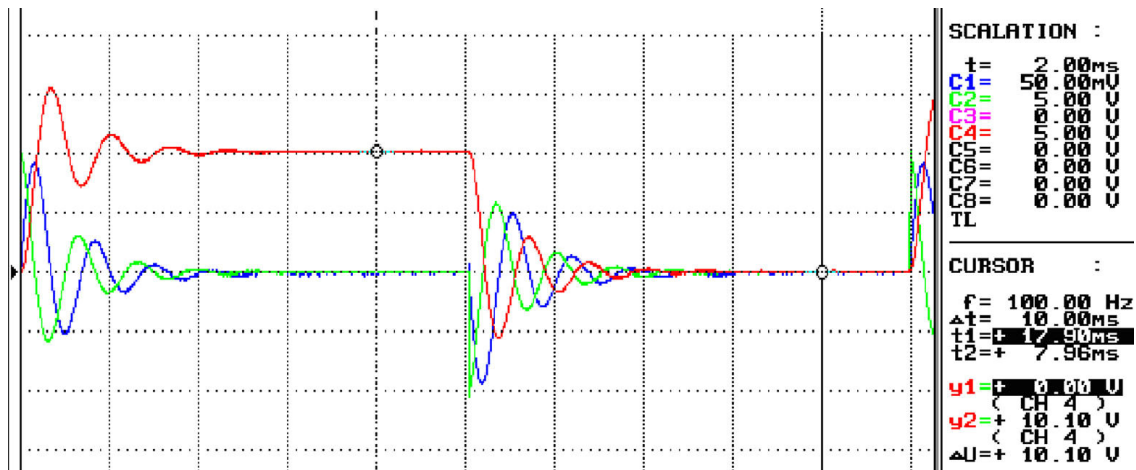
$$u_C = U_0 \left(\cos \omega_e t + \frac{\delta}{\omega_e} \sin \omega_e t \right) e^{-\delta t}$$



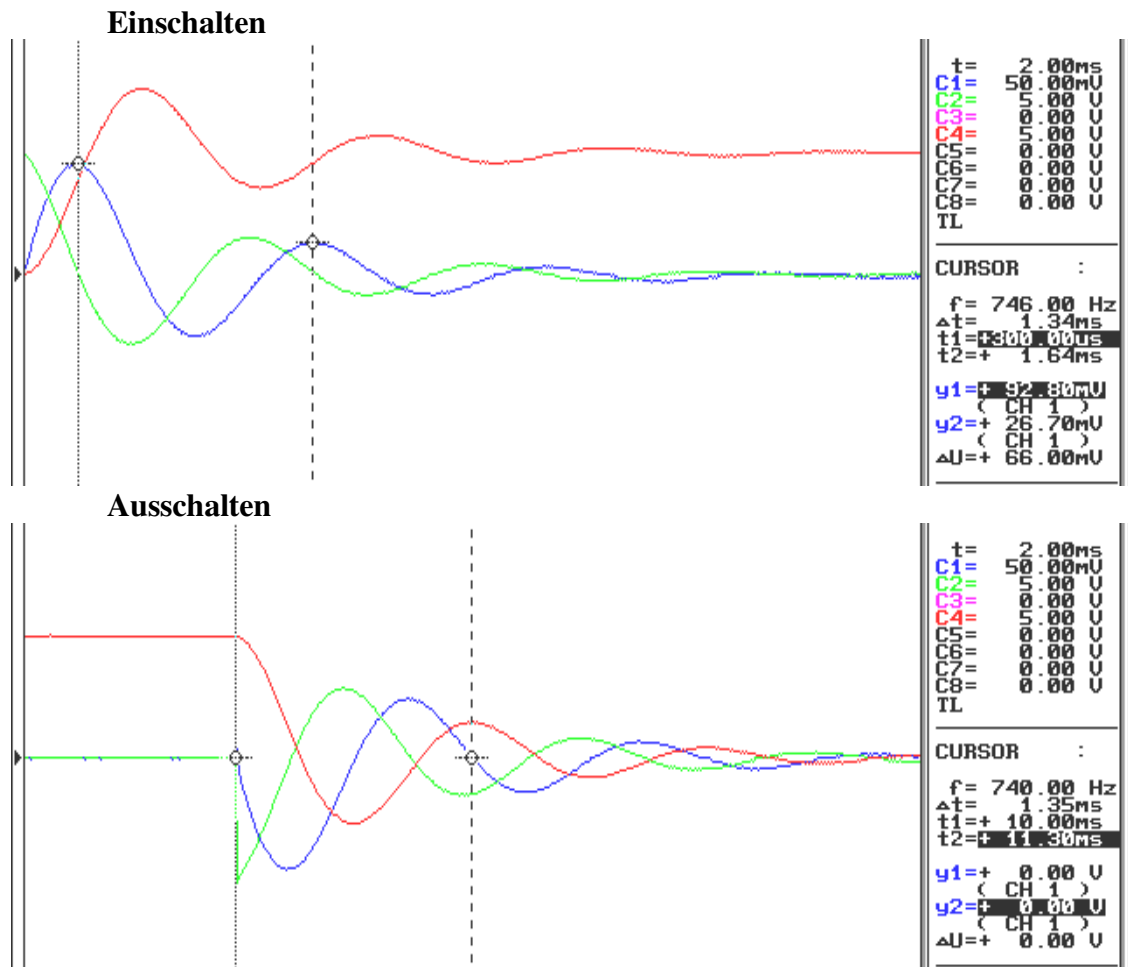

Werte aus den Messkurven:

$i_{\max 1} = 9,87 \text{ mA}$ $i_{\max 2} = 2,67 \text{ mA}$ $T_e = \Delta t = 1,35 \text{ ms}$ $U_0 = 10,1 \text{ V}$

Berechnung der Parameter aus den Messwerten: Vergleich:

$$\delta = \frac{1}{T_e} \ln \frac{i_{\max 1}}{i_{\max 2}} = 965 \text{ 1/s}$$

$$\omega_e = \frac{2\pi}{T_e} = 4654 \text{ 1/s} \Rightarrow 740 \text{ Hz}$$

$$\omega_0 = \sqrt{\omega_e^2 + \delta^2} = 4753 \text{ 1/s} \Rightarrow 756 \text{ Hz}$$

$$L = \frac{U_0}{\omega_e i_{\max 1}} \sqrt{\frac{i_{\max 2}}{i_{\max 1}}} = 160 \text{ mH} \quad 300 \text{ mH bei 50 Hz}$$

$$C = \frac{1}{\omega_0^2 L} = 0,27 \text{ }\mu\text{F} \quad 0,22 \text{ }\mu\text{F}$$

$$R = \delta \cdot 2L = 308 \text{ }\Omega \quad 300 \text{ }\Omega$$

2. Aperiodischer Grenzfall (R=1600 Ω)

Theorie:

$$i = \frac{2U_0}{R} \delta t e^{-\delta t} \quad i = -\frac{2U_0}{R} \delta t e^{-\delta t}$$

$$u_R = U_0 \cdot 2 \delta t e^{-\delta t} \quad u_R = -U_0 \cdot 2 \delta t e^{-\delta t}$$


$$u_L = U_0(1 - \delta t)e^{-\delta t}$$

$$u_L = -U_0(1 - \delta t)e^{-\delta t}$$


$$u_C = U_0 - U_0(1 + \delta t)e^{-\delta t}$$

$$u_C = U_0(1 + \delta t)e^{-\delta t}$$

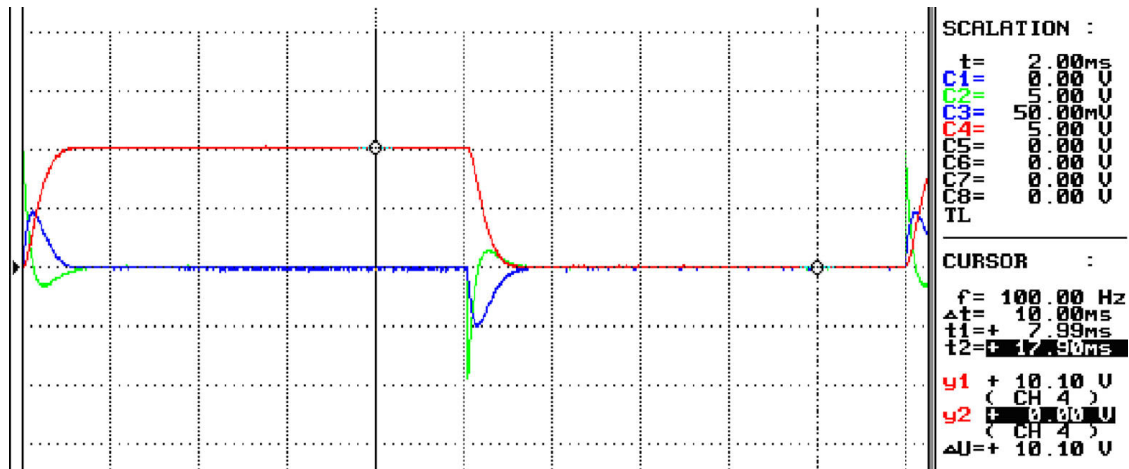
mit $\delta^2 = (R/2L)^2 = \omega_0^2 = 1/LC$ und $\omega_e = 0$



Einschalten

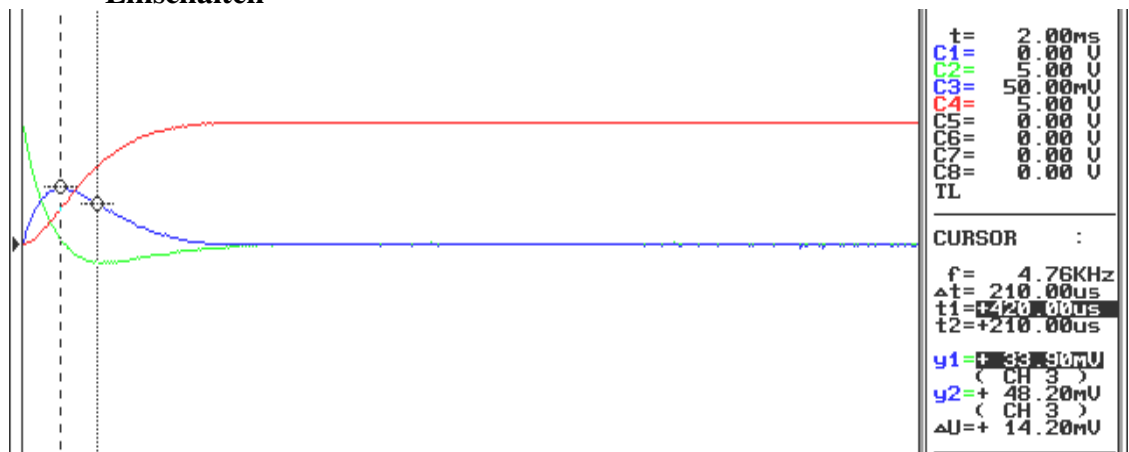

Ausschalten

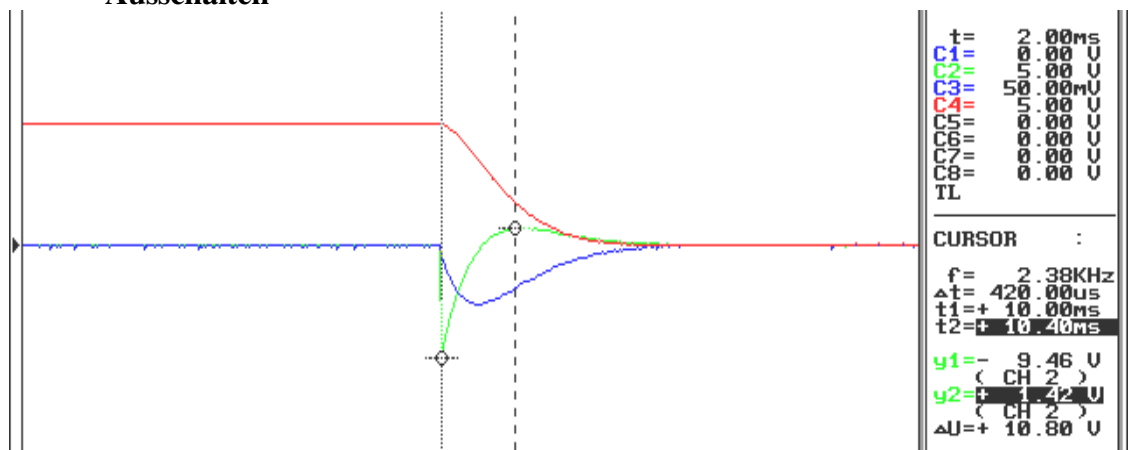

Werte aus den Messkurven:

$$i_{\max} = 4,82 \text{ mA}$$

$$t_{\max} = \Delta t = 210 \text{ } \mu\text{s}$$

$$U_0 = 10,1 \text{ V}$$

Berechnung der Parameter aus den Messwerten:

$$\begin{aligned} \delta &= 1/t_{\max} = \omega_0 = 4\,761\,1/\text{s} \Rightarrow 757\text{ Hz} \\ R &= 2U_0/i_{\max} e = 1\,541\ \Omega \\ L &= R/2\delta = 160\text{ mH} \\ C &= 1/\delta^2 L = 0,27\ \mu\text{F} \end{aligned}$$

Vergleich:

$$\begin{aligned} &1\,600\ \Omega \\ &300\text{ mH bei } 50\text{ Hz} \\ &0,22\ \mu\text{F} \end{aligned}$$

3. Aperiodischer Fall (R=5000 Ω)

Theorie:

$$i = \frac{U_0}{R} \frac{\delta}{\sqrt{\delta^2 - \omega_0^2}} (e^{-\delta_1 t} - e^{-\delta_2 t})$$

$$i = -\frac{U_0}{R} \frac{\delta}{\sqrt{\delta^2 - \omega_0^2}} (e^{-\delta_1 t} - e^{-\delta_2 t})$$

$$u_R = U_0 \frac{\delta}{\sqrt{\delta^2 - \omega_0^2}} (e^{-\delta_1 t} - e^{-\delta_2 t})$$

$$u_R = -U_0 \frac{\delta}{\sqrt{\delta^2 - \omega_0^2}} (e^{-\delta_1 t} - e^{-\delta_2 t})$$



$$u_L = \frac{U_0}{2\sqrt{\delta^2 - \omega_0^2}} (\delta_2 e^{-\delta_2 t} - \delta_1 e^{-\delta_1 t})$$

$$u_L = \frac{-U_0}{2\sqrt{\delta^2 - \omega_0^2}} (\delta_2 e^{-\delta_2 t} - \delta_1 e^{-\delta_1 t})$$


$$u_C = \frac{U_0}{2\sqrt{\delta^2 - \omega_0^2}} [\delta_1 (e^{-\delta_2 t} - 1) + \delta_2 (1 - e^{-\delta_1 t})]$$

$$u_C = \frac{U_0}{2\sqrt{\delta^2 - \omega_0^2}} [\delta_2 e^{-\delta_1 t} - \delta_1 e^{-\delta_2 t}]$$

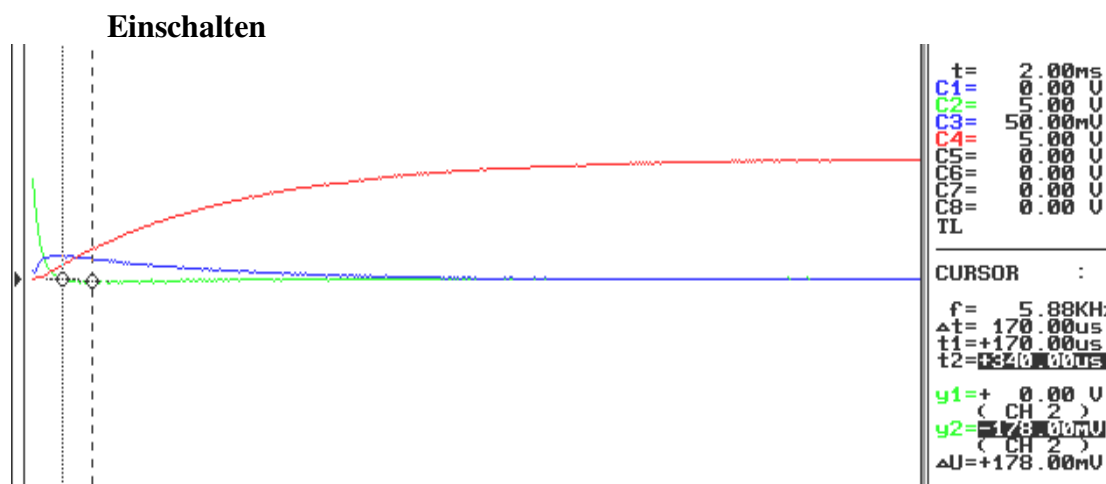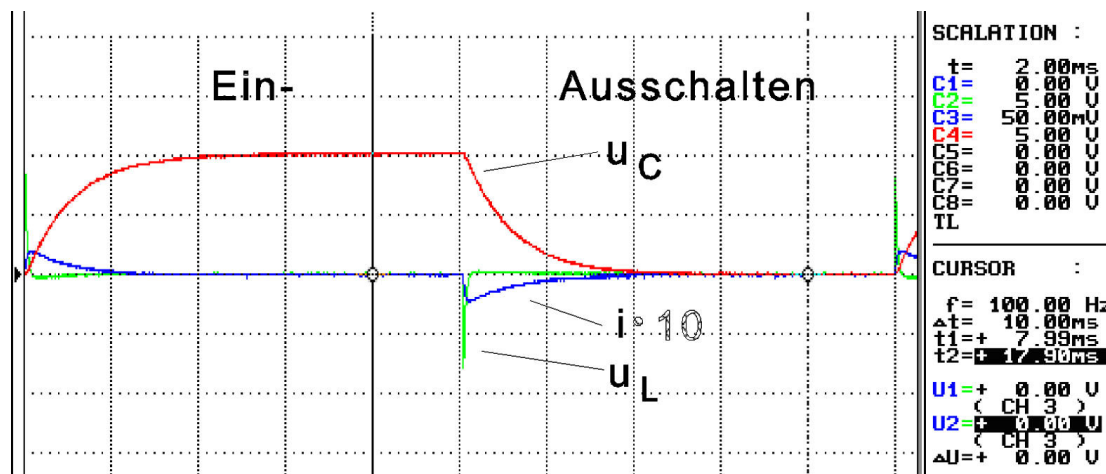mit $\delta_{1/2} = \delta \mp \sqrt{\delta^2 - \omega_0^2}$ oder $\tau_{1/2} = 1/\delta_{1/2}$, $\delta = R/2L$ und $\omega_0^2 = 1/LC$



Ausschalten

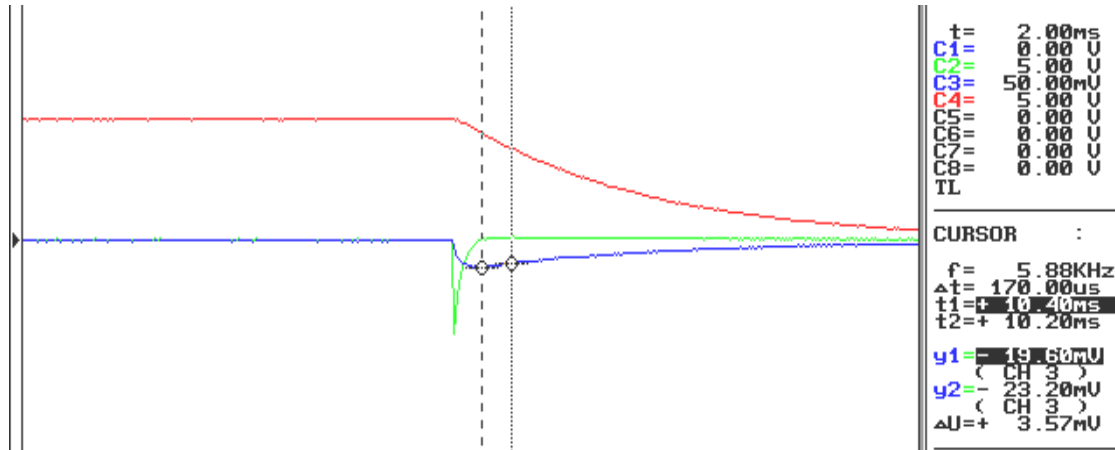

Werte aus den Messkurven: $i_{\max 1} = 2,32 \text{ mA}$ $t_{\max} = 170 \text{ } \mu\text{s}$ $U_0 = 10,1 \text{ V}$
 $i_{\max 2} = 1,96 \text{ mA}$ $u_{L\max 2} = -178 \text{ mV}$

Berechnung der Parameter aus den Messwerten:

Vergleich:

$$\delta = \frac{1}{2t_{\max}} \ln \frac{U_0}{-u_{L\max 2}} = 11\,900 \text{ 1/s}$$

$$R = \frac{i_{\max 2} U_0}{i_{\max 1}^2} = 3\,700 \text{ } \Omega$$

5 000 Ω

$$L = R/2\delta = 160 \text{ mH}$$

300 mH bei 50 Hz

$$C = \frac{i_{\max 1}^2 L}{-u_{L\max 2} U_0} = 0,48 \text{ } \mu\text{F}$$

0,22 μF

$$\omega_0 = 1/\sqrt{LC} = 3\,600 \text{ 1/s} \Rightarrow 575 \text{ Hz}$$

(Genauigkeit: Beachte, dass 1 Bildpunkt = 178 mV bzw. 1,7 mV ist!)